

CONTACTLESS IC CARD 501	Slot2	O(2)	X(4)
CONTAC	Slot1	X(1)	(2)
	·	Slot1	Slot2
		CONTACT LESS IC	CARD 502

 $\times$  = COLLISION  $\bigcirc$  = NO COLLISION

	<del></del>	<del>,</del>	T				
CONTACTLESS IC CARD 601	Slot1 Slot2	NO JUDGMENT	O(4)	(8)	X(12)	X(16)	
		JUDGMENT	(6)()	(2)()	X(11)	X(15)	
CONTACTLES		NO JUDGMENT	(2)	(9) ×	(10)	O(14)	
		JUDGMENT	<u>X(1)</u>	(5)	(6)()	O(13)	
			JUDGMENT	NO JUDGMENT	JUDGMENT	NO JUDGMENT	
			Slot1		Slot2		
			CONTACT LESS IC CARD 602				

 $\times$  = COLLISION  $\bigcirc$  = NO COLLISION

		ENT	_	
CONTACTLESS IC CARD 701	Slot1 Slot2	NO JUDGMENT	O(4)	(8)×
		JUDGMENT *	O(3)	<u>x(7)</u>
		NO JUDGMENT	×(2)	(9)()
		JUDGMENT ★	O(1)	O(5)
			Slot1	Slot2
			CONTACT LESS IC CARD 702	

 $\times$  = COLLISION  $\bigcirc$  = NO COLLISION

	<u> </u>	Γ	Γ	1	
01	Slot4	O(4)	O(8)	O(12)	×(16)
S IC CARD 8	Slot3	O(3)	(7)0	×(11)	O(15)
CONTACTLESS IC CARD 801	Slot2	O(2)	(9) ×	O(10)	O(14)
CC	Slot1	×(1)	O(5)	(6)()	O(13)
		Slot1	Slot2	Slot3	Slot4
		CONTACT LESS IC CARD 802			


 $\times$ =COLLISION  $\bigcirc$ =NO COLLISION


	3 Slot4	NO JUDGMENT NO JUDGMENT	O(6) O(7) O(8)	O(14) O(15) O(16)	O(22) O(23) O(24)	O(30) O(31) O(32)	O(38) O(39) O(40)	<u>x(46)</u> O(47) O(48)	O(54) × (55) × (56)	O(62) × (63) × (64)
CONTACTLESS IC CARD 901	Slot3	JUDGMENT	O(5)	O(13)	O(21)	O(29)	×(37)	O(45)	O(53)	O(61)
NTACTLES	Slot2	NO	O(4)	O(12)	O(20)	× (28)	O(36)	O(44)	O(52)	(09)O
COJ	Sk	JUDGMENT	O(3)	O(11)	×(19)	O(27)	O(35)	O(43)	O(51)	O(59)
	ot 1	NO JUDGMENT	O(2)	×(10)	O(18)	O(26)	O(34)	O(42)	O(50)	O(58)
	Slot1	JUDGMENT	×(1)	(6)()	O(17)	O(25)	O(33)	O(41)	O(49)	O(57)
			Slot1 JUDGMENT	NO JUDGMENT	Slot2 JUDGMENT	NO JUDGMENT	Slot3 JUDGMENT	NO JUDGMENT	Slot4 JUDGMENT	NO JUDGMENT
			Slot1 Slot3							
			CONTACTLESS IC CARD 902							


 $X = COLLISION \bigcirc = NO COLLISION$ 


	t4	NO JUDGMENT	O(8)	O(16)	O(24)	×(32)
001	t3 Slot4	JUDGMENT	O(7)	O(15)	O(23)	× (31)
		NO JUDGMENT	(9)O	O(14)	×(22)	O(30)
SIC CARD	Slot2 Slot3	JUDGMENT ★	O(5)	O(13)	O(21)	O(29)
CONTACTLESS IC CARD 1001		NO JUDGMENT	O(4)	×(12)	O(20)	O(28)
CON		JUDGMENT ★	O(3)	O(11)	O(19)	O(27)
		NO JUDGMENT	×(2)	O(10)	O(18)	O(26)
	Slot1	JUDGMENT ★	O(1)	(6)O	(71)0	O(25)
			Slot 1	Slot 2	Slot 3	Slot 4
			CONTACTLESS IC CARD 1002			

X=COLLISION O=NO COLLISION

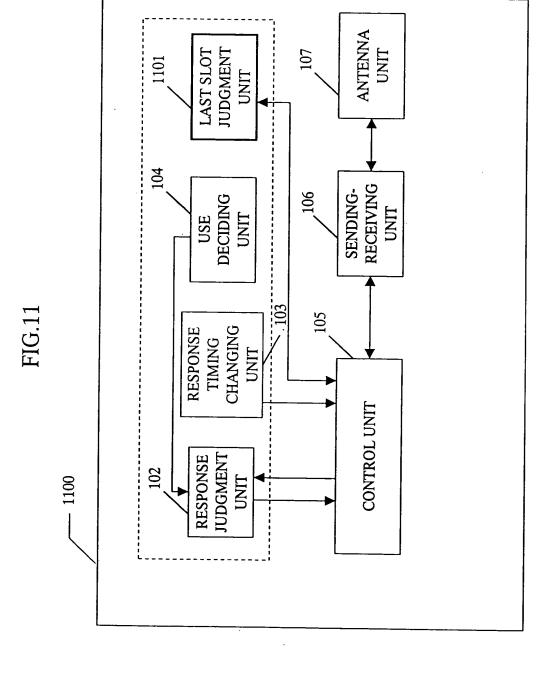


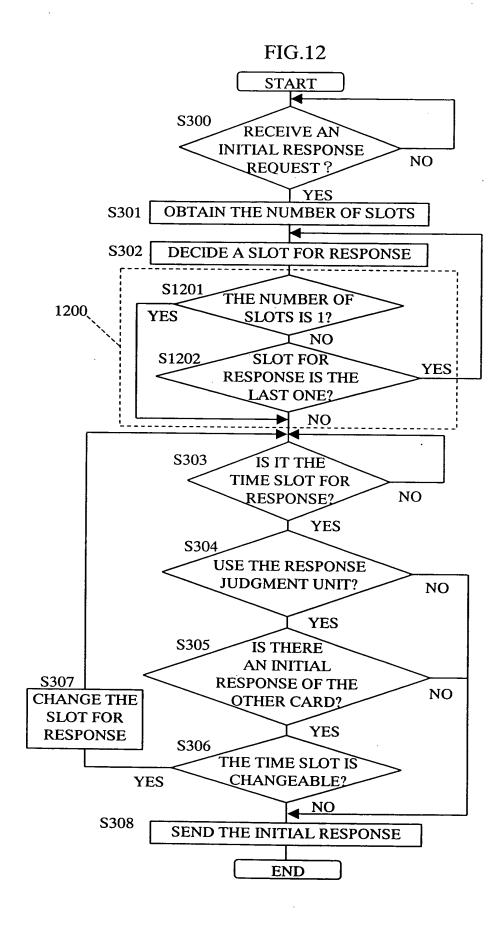

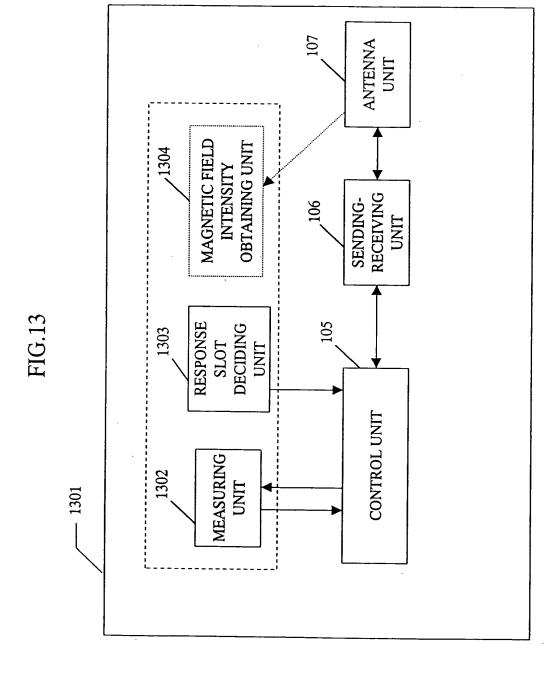

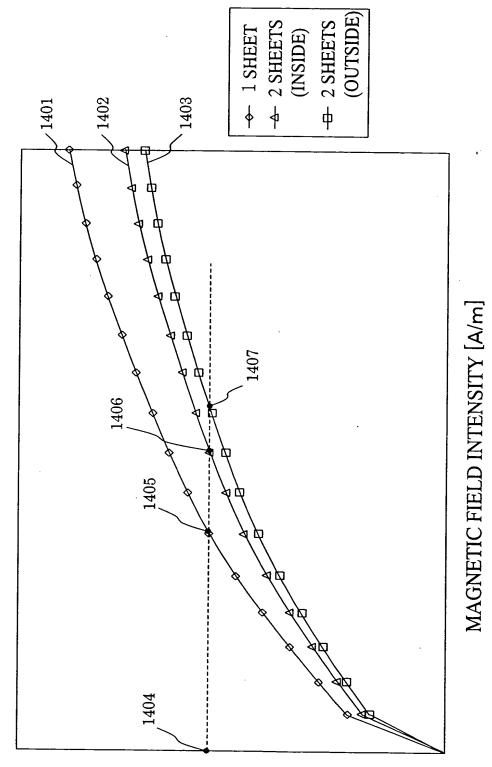

ELECTROMOTIVE FORCE (VOLTAGE) [V]

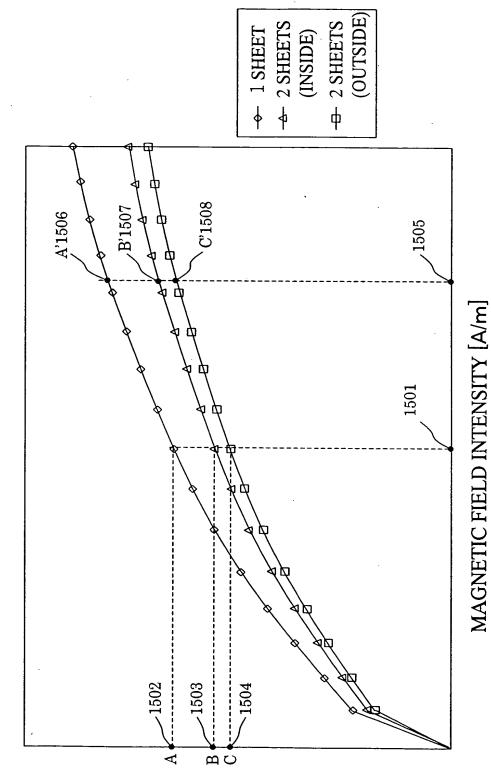

ELECTROMOTIVE FORCE (VOLTAGE) [V]

FIG.16 PRIOR ART

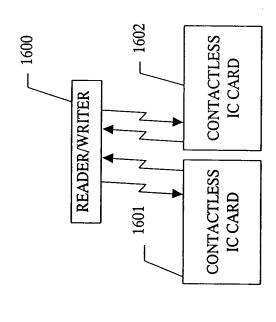


FIG.17 PRIOR ART

